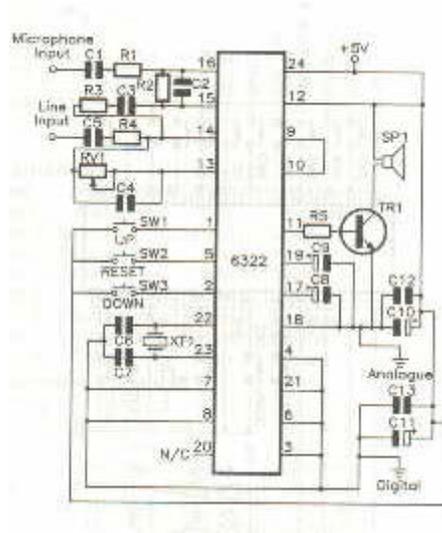


Voice Changer.

Don't ask me how this sounds as ive not built it as of yet but if anybody does please let me know.Thank's



Parts list

R1, 3, 4, 5 = 10k

R2 = 100k

Rv1 = 100k

C1, 3, 5, = 0.22uf

C2, 4, 5, 7, = 33pf

C8, 9, = 47uf 25v

C10, 11, = 10uf 50v

C12, 13, = 0.1uf 16v minidisc

TR1 = BC338

XT1 = MHZ Crystal

deano@deanwhite.freereserve.co.uk